


Assignment 4 .

classmate

Date _____

Page _____

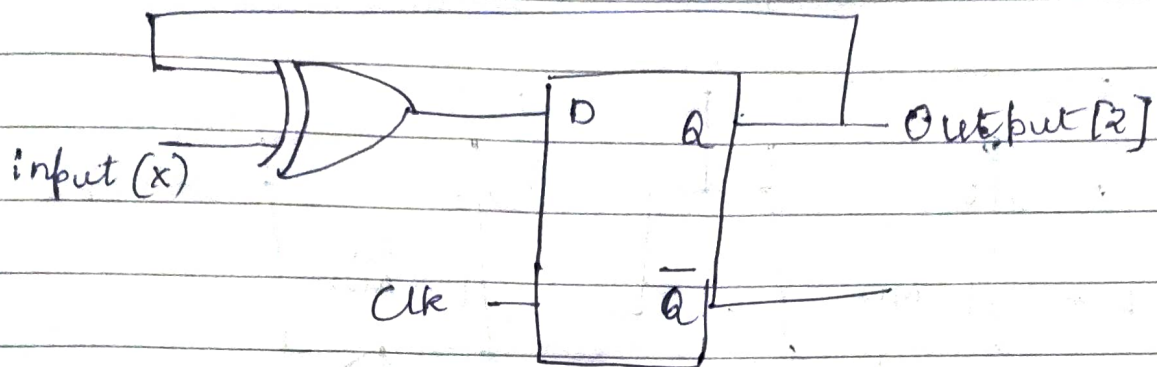1. Explain the behaviour of given circuit .



State table .

XOR gate inputs are	present (Q)	input (x)	Q _{next}
external i/p = x .	0	0	0
feedback i/p = Q .	0	1	1
	1	0	1
	1	1	0

$$D = x \oplus Q$$

$$Q_{next} = D$$

$$Q_{next} = x \oplus Q$$


$$Z_{next} = x \oplus Z$$

$$\text{Case 1 : } x = 0 : Q_{next} = Q$$

$$\text{Case 2 : } x = 1 : Q_{next} = \bar{Q}$$

Circuit is TFF .

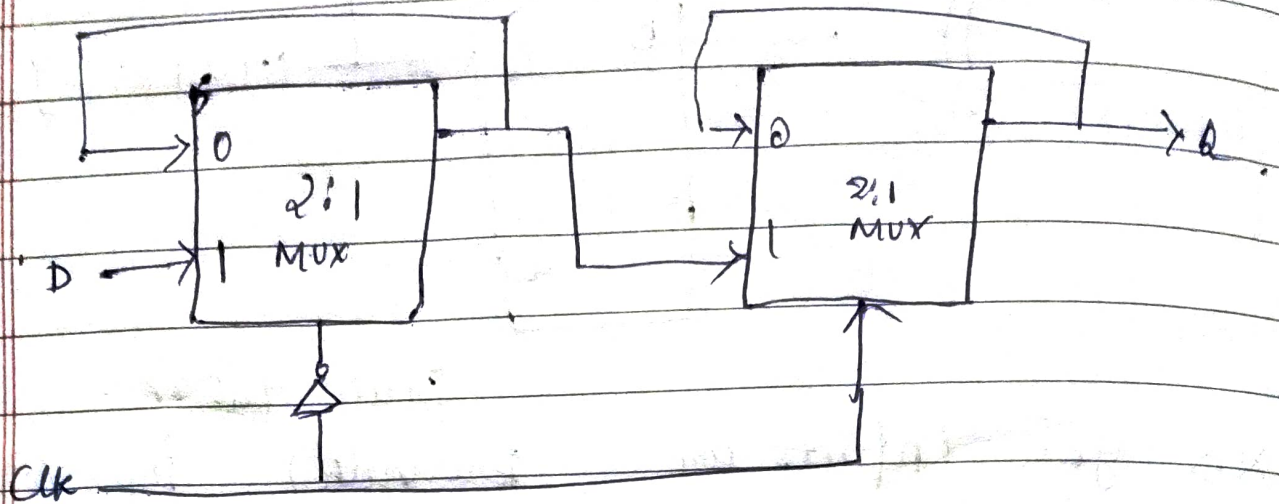2. Design a posedge triggered DFF using 2:1 Mux only.



$$Q_{next} = Clk \cdot 0 + \overline{Clk} \cdot Q$$

Operation :


Master enable = $\overline{clk}$

Slave enable = clk .

$Clk = 0$ master tracks i/p, slave holds

$Clk = 1$, master slaves copies masters output.

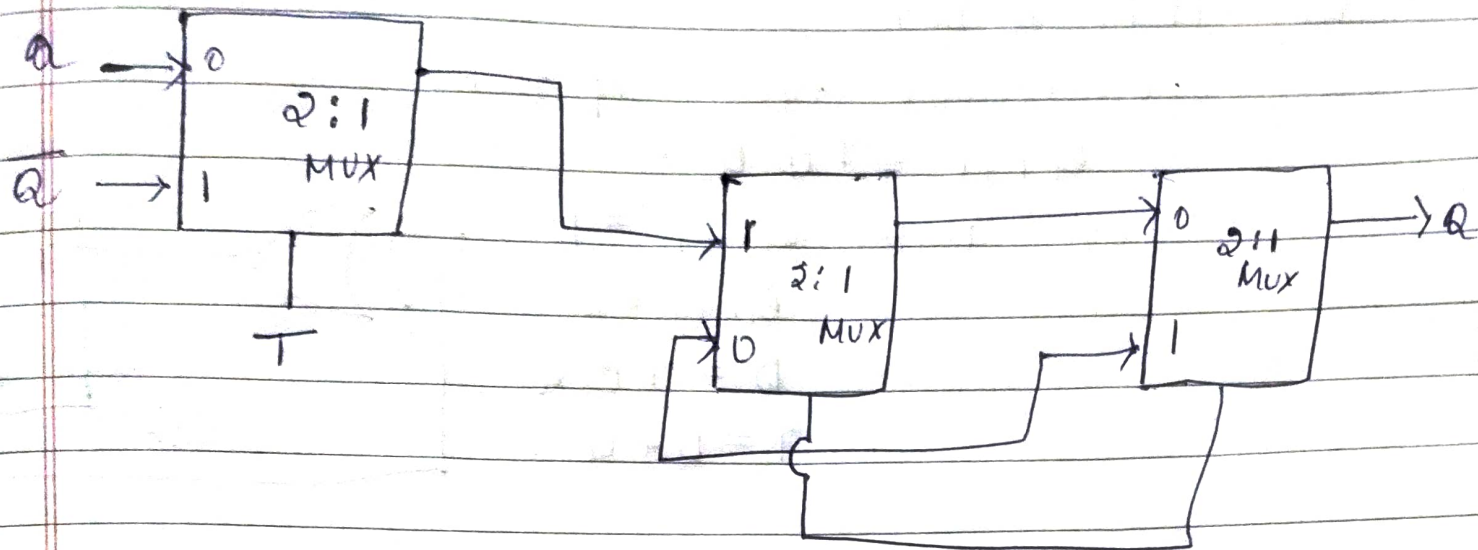3. Design a negedge triggered TFF using 2:1 MUX



4. Convert by adding external gates


a) A DFF to JKFF

Characteristic equation of JK

$$Q_{n+1} = J\bar{Q} + \bar{K}Q$$

For DFF $D = Q_{n+1}$

$$D = J\bar{Q} + \bar{K}Q$$

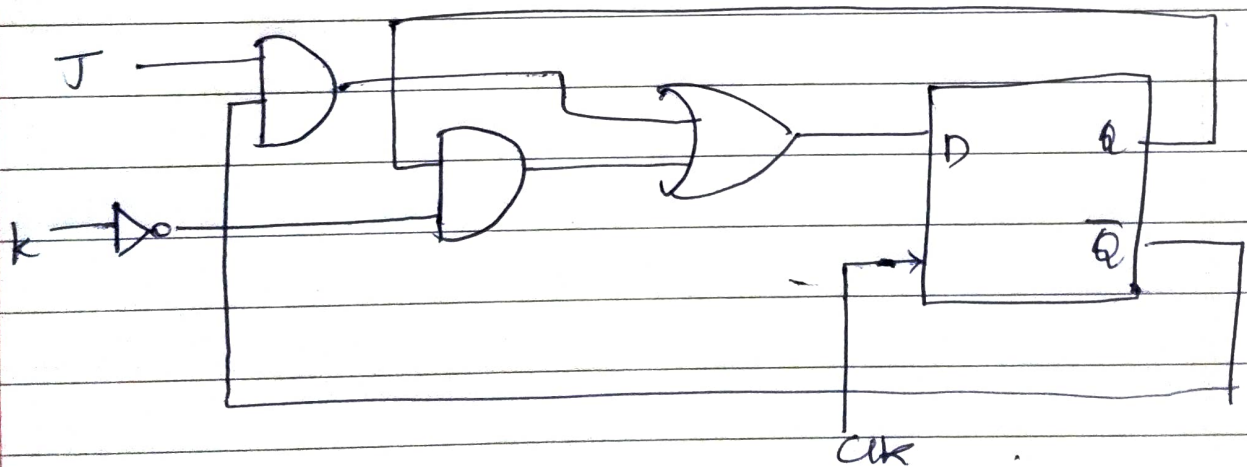

b) TFF to DFF

Characteristic eqn of TFF.

$$Q_{n+1} = T \oplus Q$$

For DFF $Q_{n+1} = D$

$$Q_{n+1} = D$$

$$D = T \oplus Q$$

$$T = D \oplus Q$$

